



MOTORCYCLE DOCTOR LLC

Craig Silvers,
Owner

PO Box 1676 / 108 N. Business Rt. 5 Camdenton, Mo 65020

Date: 06-13-17

local: (573) 346-6867 Toll Free: (888) 346-6867


web site: www.MotorcycleDoctor.com


Craig@MotorcycleDoctor.com email:

Use both wires from 2 wire plug that is connected to red fan relay. Splice + 12 volt 'Key On' wire to an extra wire going to 4 prong relay.

Positive 12 Volts from Brown/blue or Red/black

splice in extra wire

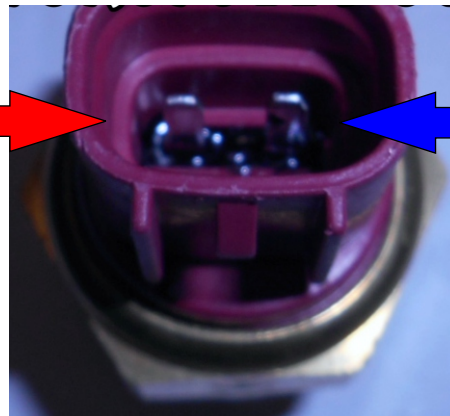


Blue wire to fan, cut 3" back  from same plug add female spade to each end.

Add Spade

Add Spade

Add Spade to new ground

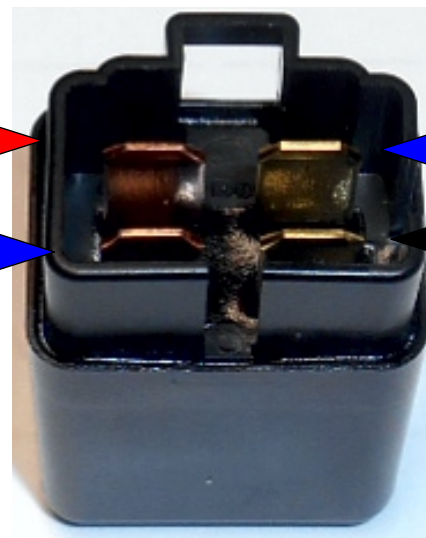

to Fan